


**AP1 - Chapter 18/20 Review**

$F_e = kq_1q_2/r^2$

= Coulomb's Law = understand how variables can change  $F_e$

DON'T plug in signs

DO draw FBD to determine direction

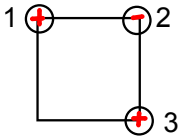

What is  $F$  on  $q_2$ ?

assume all same  $q$

Voltage	Current	Resistance	Power
•	•	•	•
•	•	•	•
•	•	•	•
•	•	•	•

Parallel	Series
multiple paths	ONE path
$1/R_t = \sum 1/R_i$ ( $R \downarrow$ )	$R_t = \sum R_i$ ( $R \uparrow$ )
$I_t = \sum I_i$	$I_t = I_i$
$V_t = V_i$	$V_t = \sum V_i$
$C_t = \sum C_i$ ( $C \uparrow$ )	$1/C_t = \sum 1/C_i$ ( $C \downarrow$ )

**Equivalent Resistance**

\*\*\*do what you know FOR SURE first

\*\*\* pay attentions to

- >  $I$ (Total) vs  $I$  (through specific resistor or path)
- >  $V$ (Total) vs  $V$  (Across ONE branch)
- >  $R$  (Total) vs  $R$  (of one part, one resistor)